


VHDL Design Labs

By Ibrahim Mezzah


<https://github.com/mezzahB>

Digital circuit design examples using Xilinx Vivado

Tools

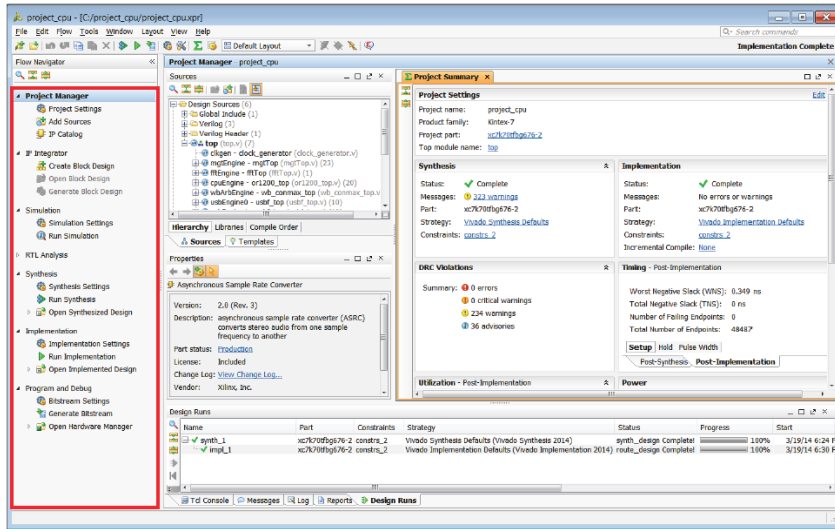

Xilinx Vivado

 


Nexys 4 DDR Board

➤ <https://www.amd.com/en/products/software/adaptive-socs-and-fpgas/vivado.html>

➤ https://reference.digilentinc.com/_media/nexys4-ddr:nexys4ddr_rm.pdf

Digital circuit design examples using Xilinx Vivado


FPGA Based Design Flow

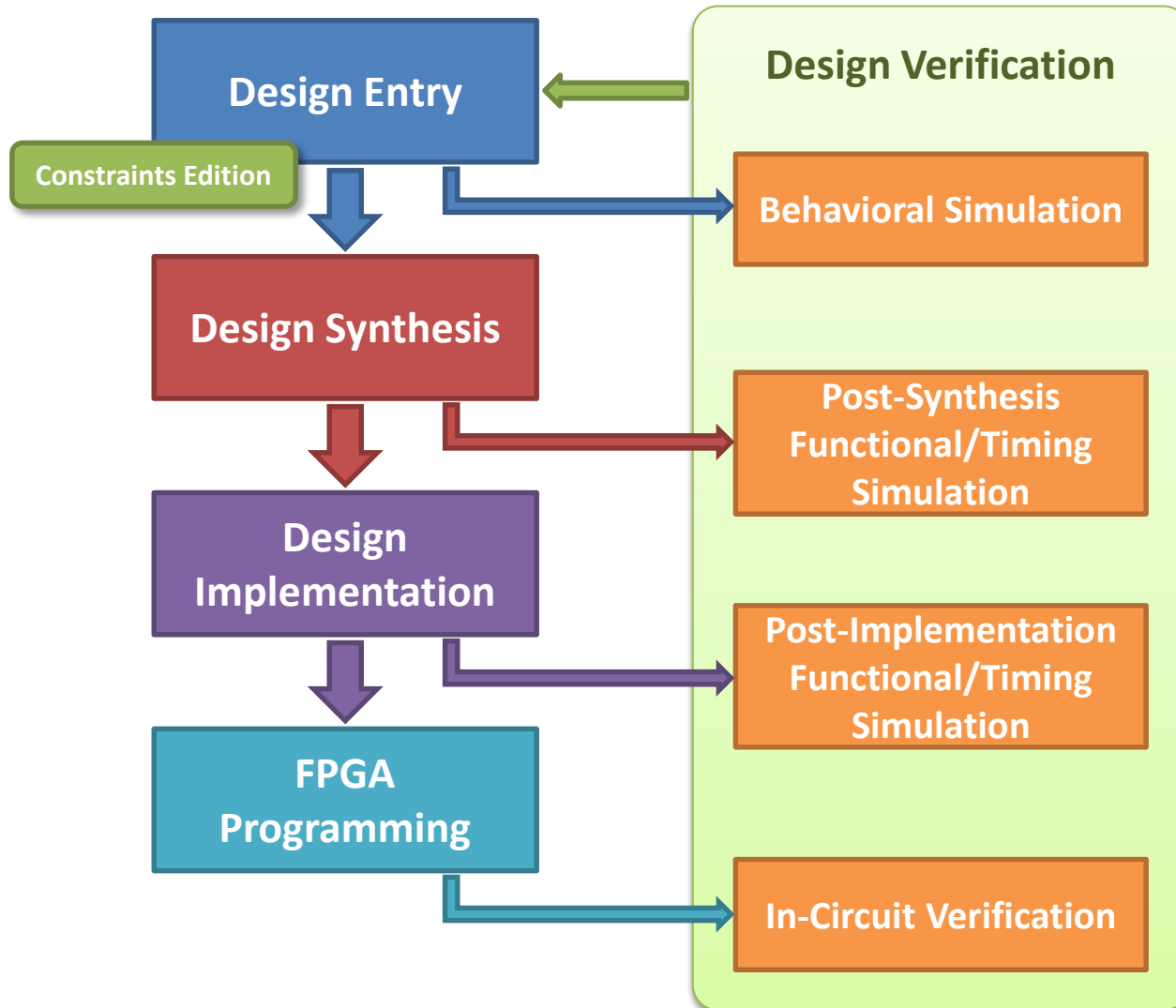

Digital circuit design examples using Xilinx Vivado

Simulation


Testbench

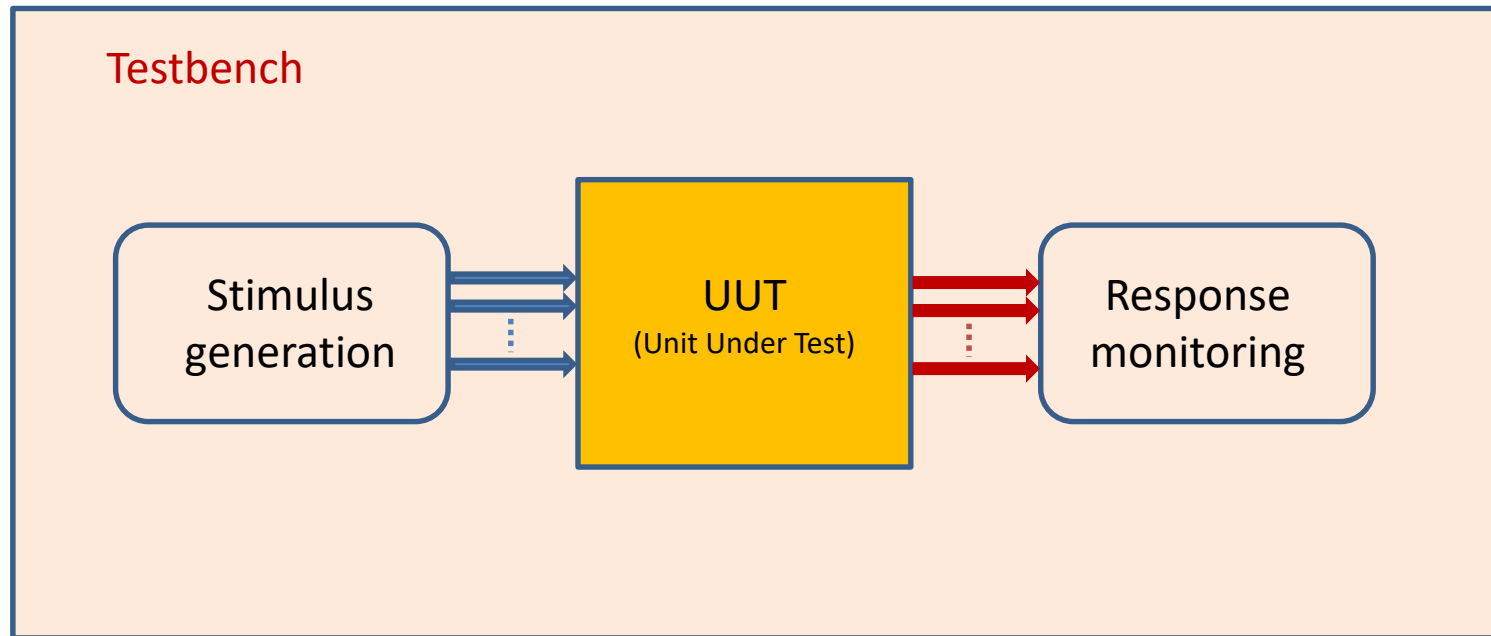

Digital circuit design examples using Xilinx Vivado

Design 0

Adder 1 bit

 

With Carry_in

Without Carry_in


A	B	S	Carry_out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

A	B	Carry_in	S	Carry_out
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

Digital circuit design examples using Xilinx Vivado

Design 0

Adder 1 bit

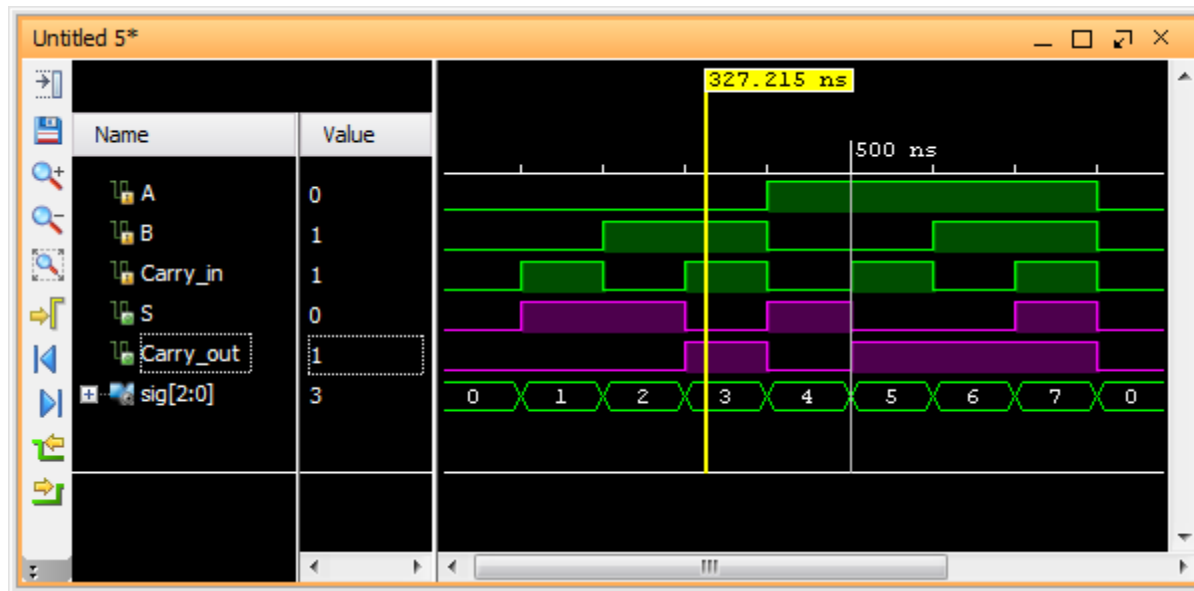


Simulation

Digital circuit design examples using Xilinx Vivado

Design 0



Adder n bit

 

Digital circuit design examples using Xilinx Vivado

Design 1


Seven Segment Display (One digit)

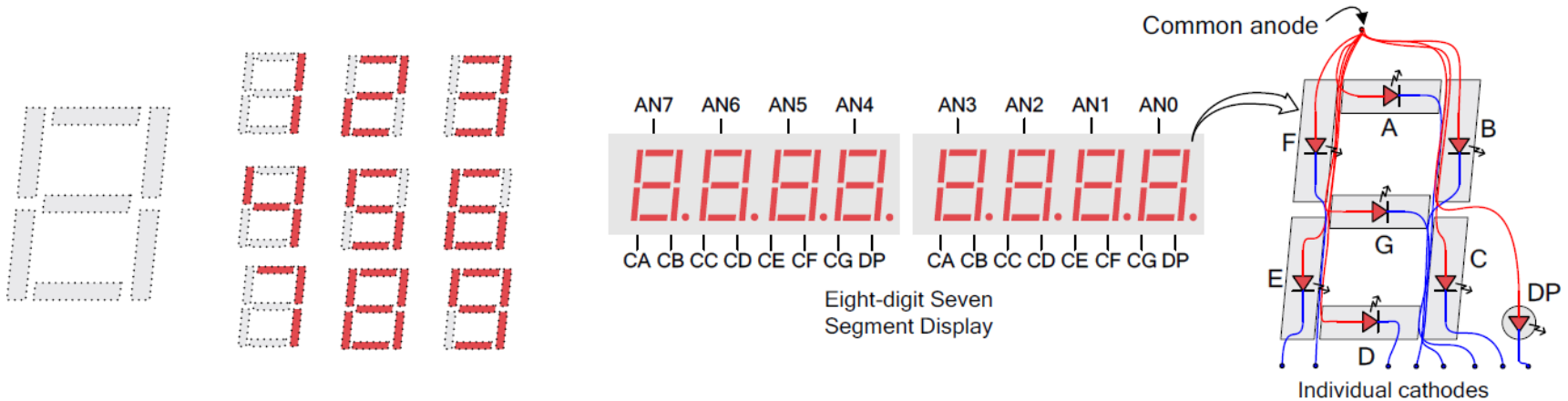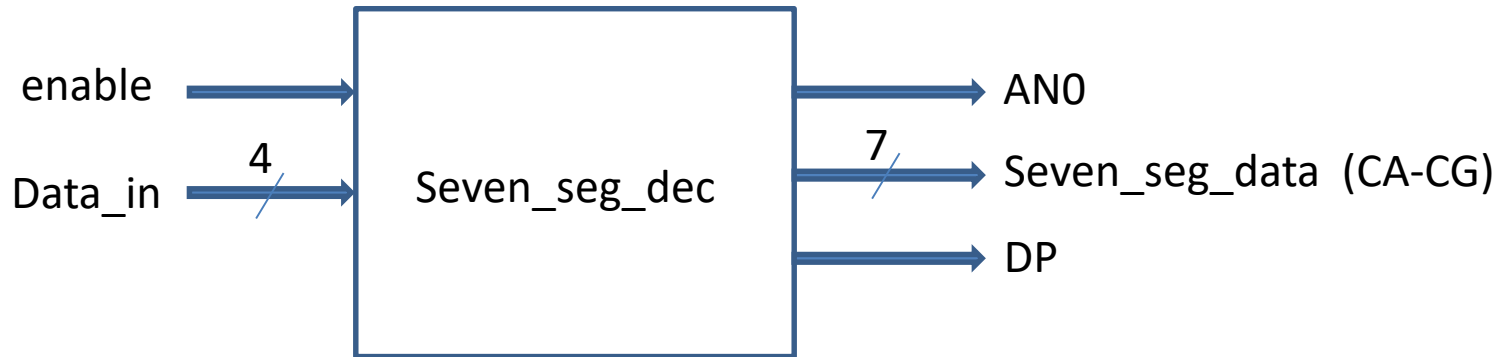

Digital circuit design examples using Xilinx Vivado

Design 1

Seven Segment Display (One digit)

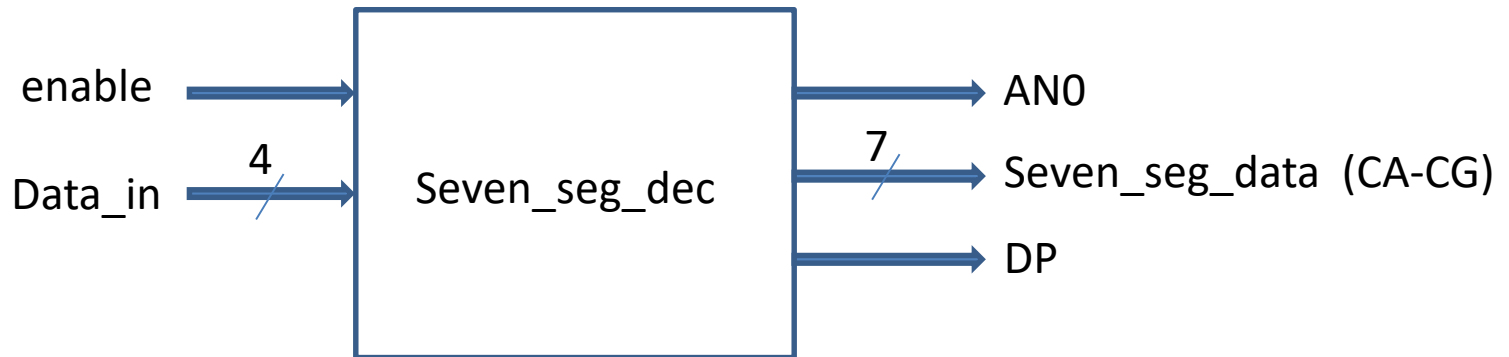


```
with BCD_IN select
  SSEG <= "0000001" when "0000",  -- 0
          "1001111" when "0001",  -- 1
          "0010010" when "0010",  -- 2
          "0000110" when "0011",  -- 3
          "1001100" when "0100",  -- 4
          "0100100" when "0101",  -- 5
          "0100000" when "0110",  -- 6
          "0001111" when "0111",  -- 7
          "0000000" when "1000",  -- 8
          "0000100" when "1001",  -- 9
          "0001000" when "1010",  -- A
          "1100000" when "1011",  -- b
          "0110001" when "1100",  -- C
          "1000010" when "1101",  -- d
          "0110000" when "1110",  -- E
          "0111000" when "1111",  -- F
          "1111111" when others;  -- turn off all LEDs
```

Digital circuit design examples using Xilinx Vivado

Design 1

Seven Segment Display (One digit)

 


Design 1 implementation

Digital circuit design examples using Xilinx Vivado

Design 2

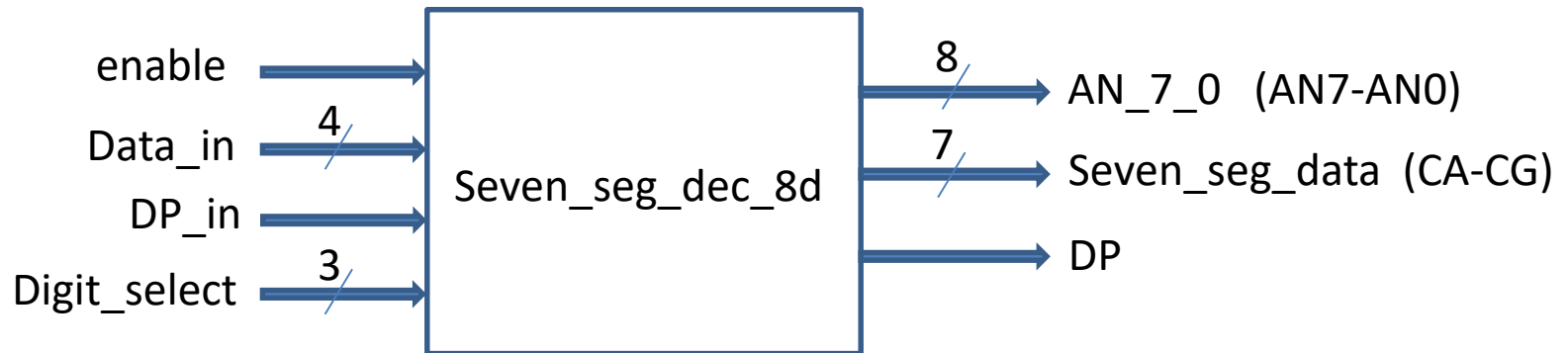Seven Segment Display (One selected digit)




Digit_select = 0 --> select digit 0

Digit_select = 1 --> select digit 1

⋮


Digit_select = 7 --> select digit 7

 

Digital circuit design examples using Xilinx Vivado

Design 2

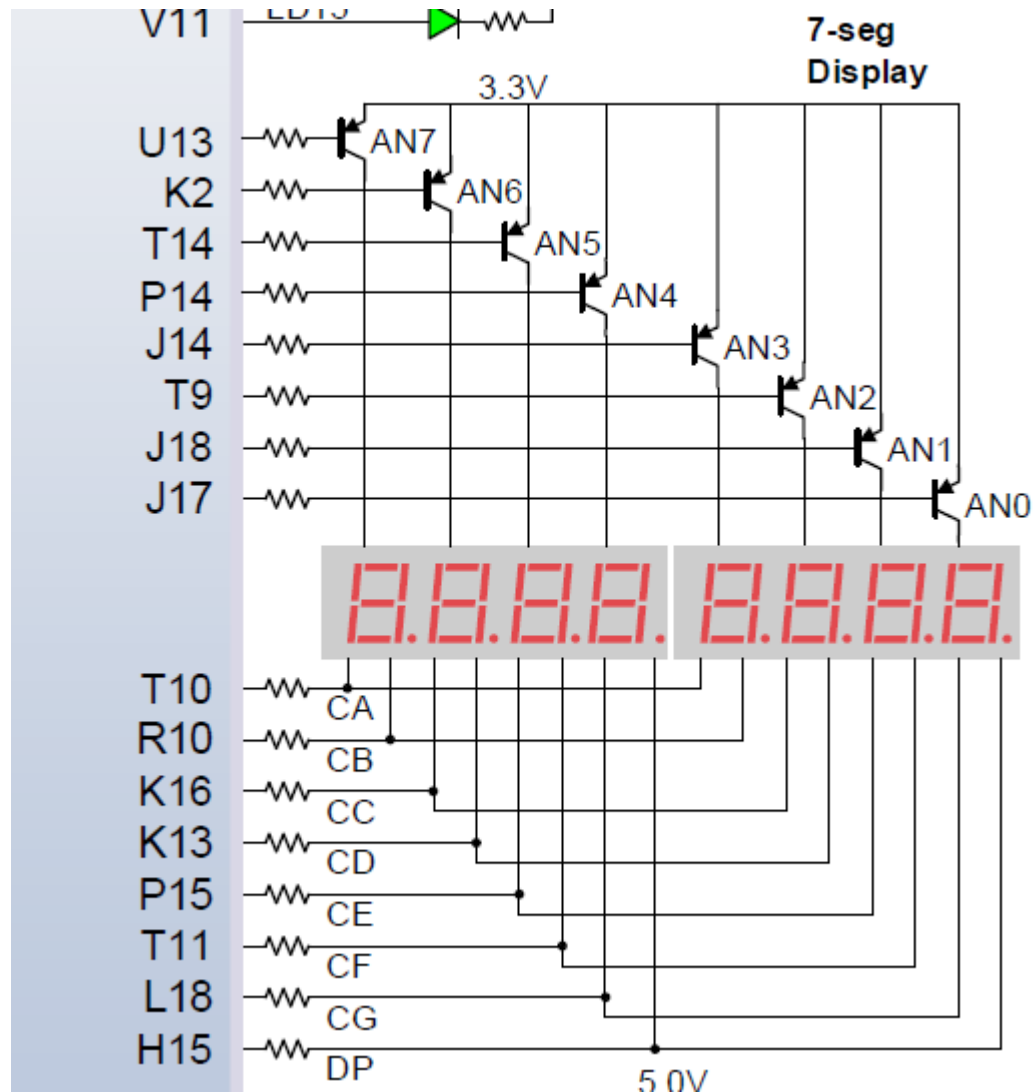
Seven Segment Display (One selected digit)



Digital circuit design examples using Xilinx Vivado

Design 2

 Seven Segment Display (One selected digit)





Design 2 implementation


Digital circuit design examples using Xilinx Vivado

Design 3

Seven Segment Display (Date display)

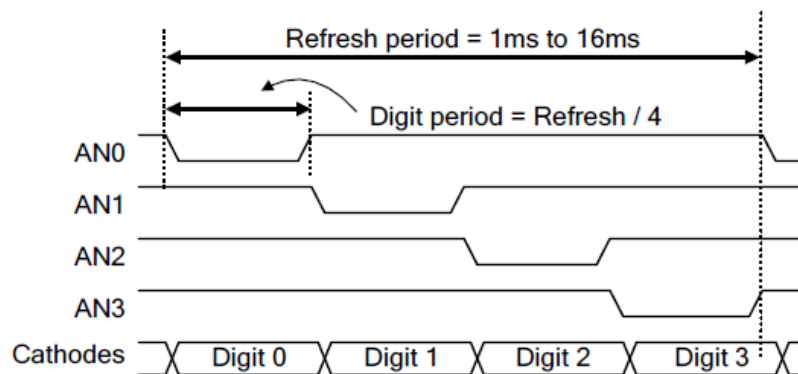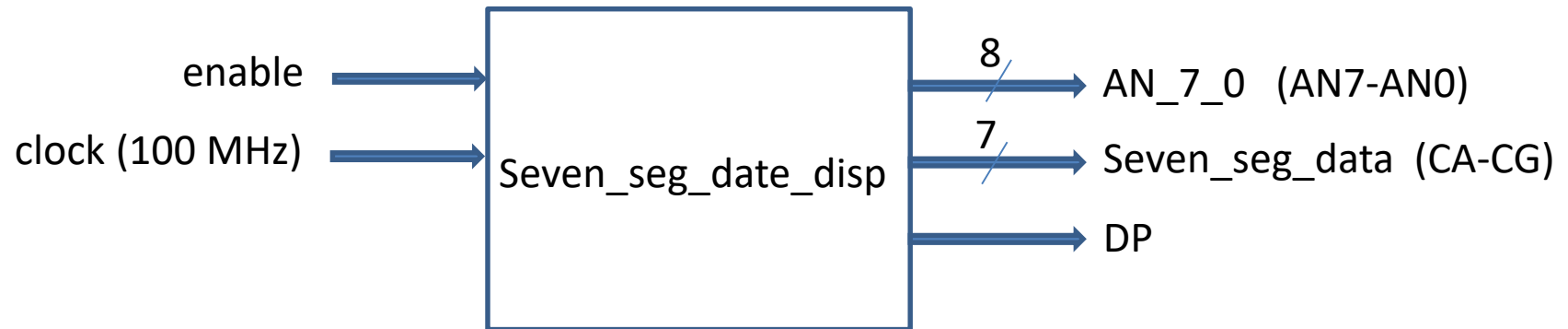

 Four digit scanning display controller timing diagram.




Display example:

16.03.2016

Digital circuit design examples using Xilinx Vivado

Design 3

Seven Segment Display (Date display)

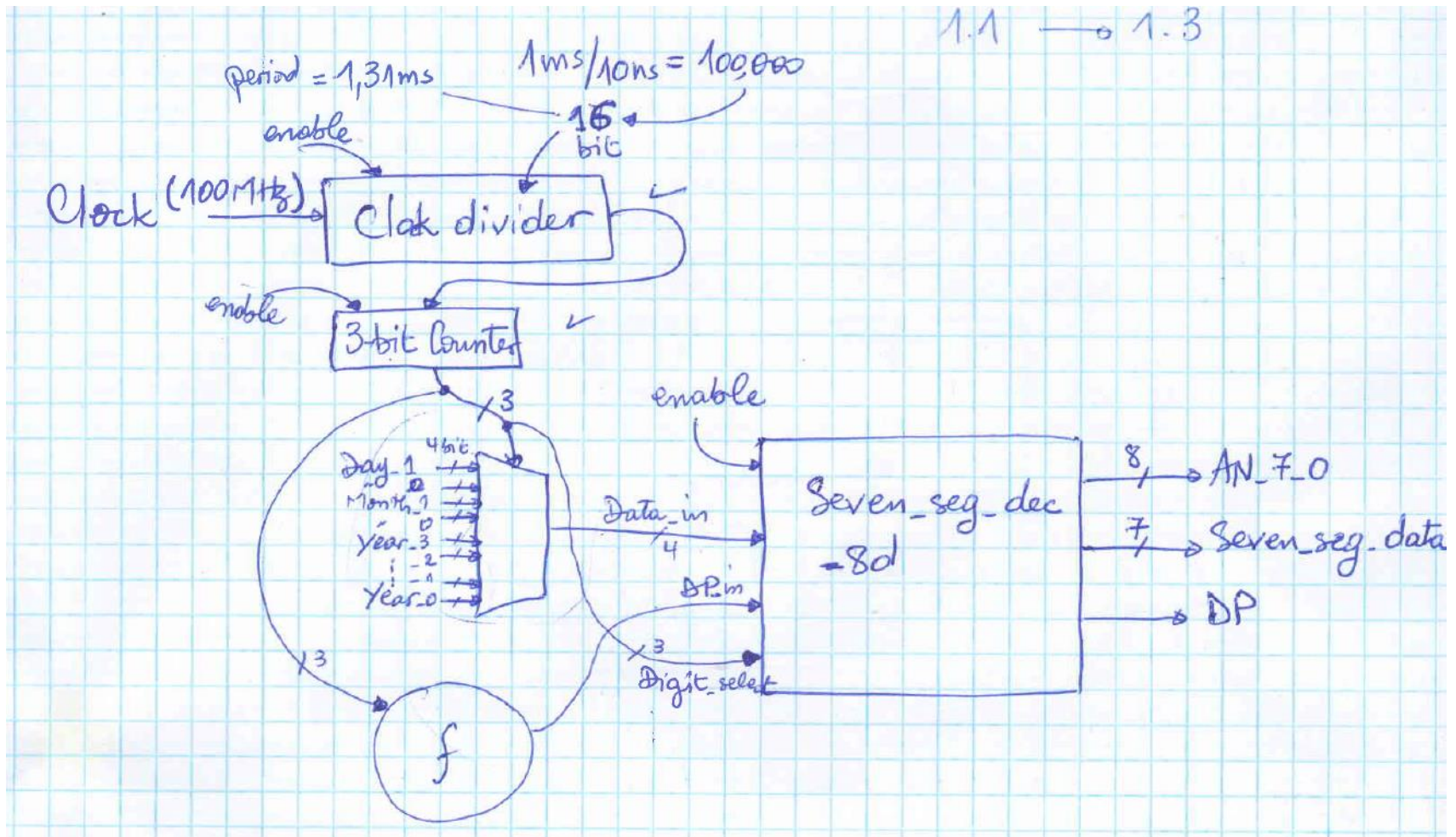

Proposed internal architecture

Digital circuit design examples using Xilinx Vivado

Design 3

Seven Segment Display (Date display)




Design 3 implementation

Digital circuit design examples using Xilinx Vivado

Design 4

Universal Asynchronous Receiver Transmitter (UART)

Transmission part

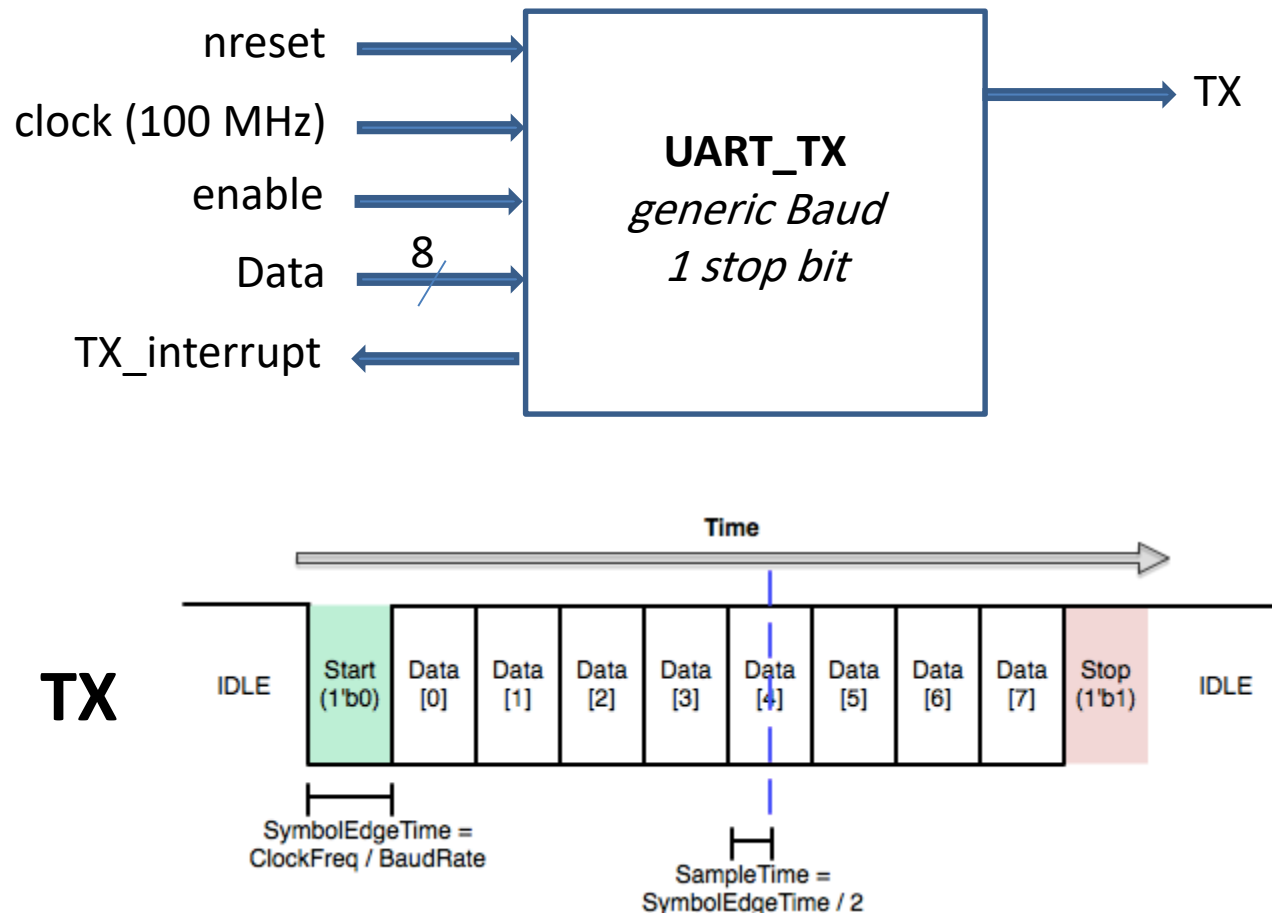


110 baud
300 baud
1 200 baud
2 400 baud
4 800 baud
9 600 baud
19 200 baud
38 400 baud
57 600 baud
115 200 baud
230 400 baud
460 800 baud
921 600 baud
1 843 200 baud
3 686 400 baud
1 baud = 1 bit/s

Digital circuit design examples using Xilinx Vivado

Design 4

Universal Asynchronous Receiver Transmitter (UART)

Transmission part

 


Shift register functioning

Digital circuit design examples using Xilinx Vivado

Design 4

Universal Asynchronous Receiver Transmitter (UART)


Transmission part

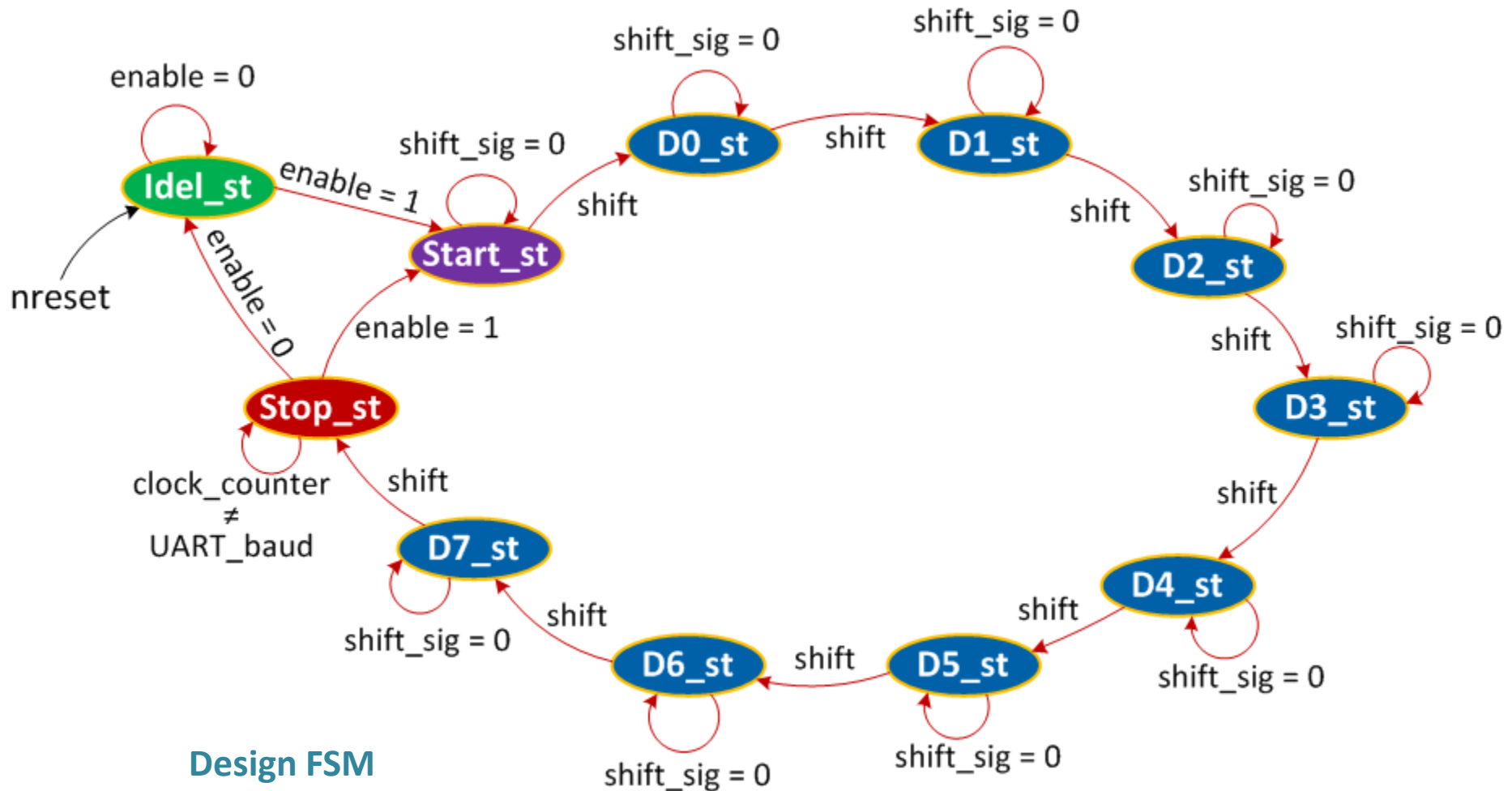

Digital circuit design examples using Xilinx Vivado

Design 4

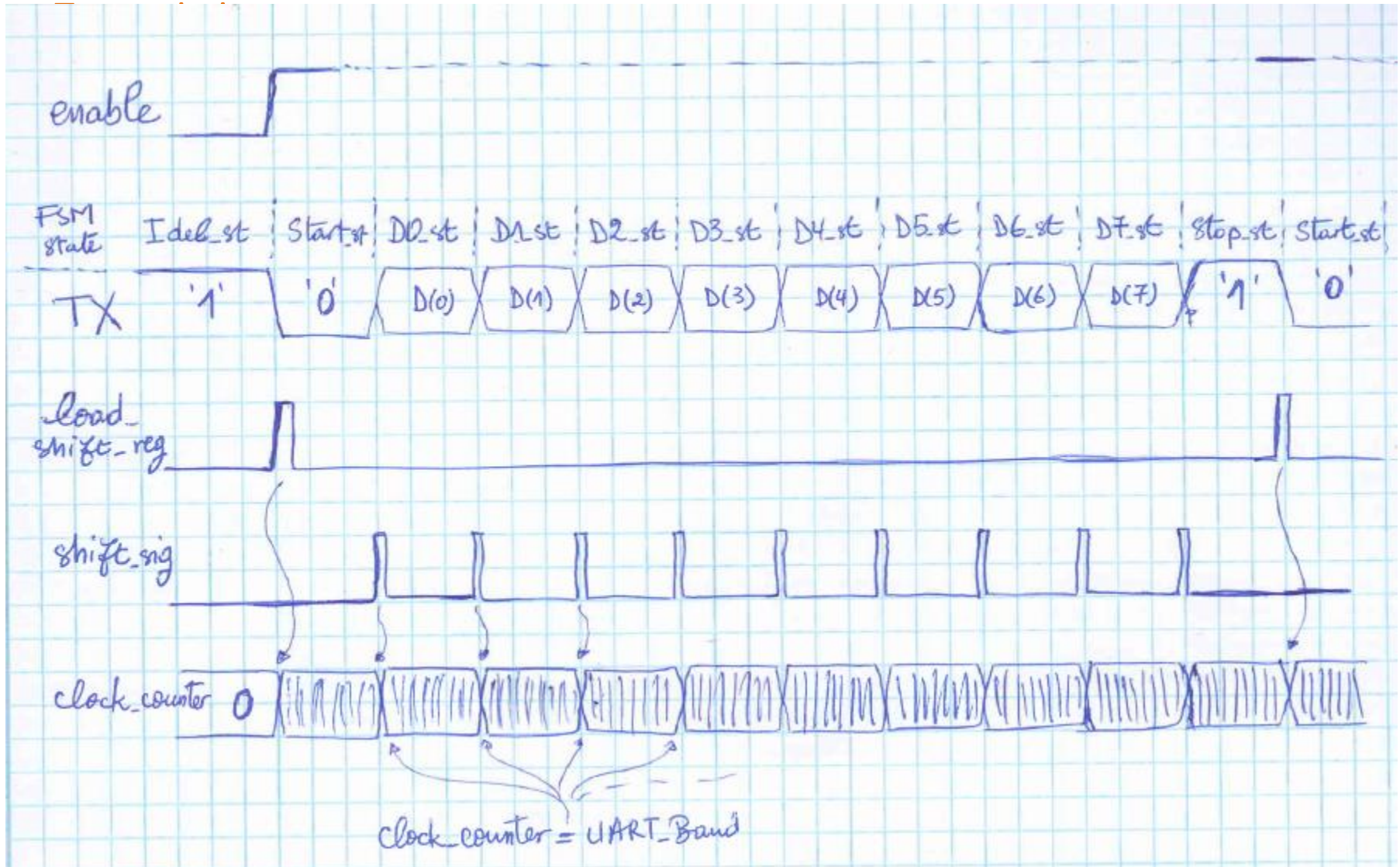Universal Asynchronous Receiver Transmitter (UART)




Digital circuit design examples using Xilinx Vivado

Design 4

Universal Asynchronous Receiver Transmitter (UART)

Transmission part

 


Simulation

Digital circuit design examples using Xilinx Vivado

Design 5

Universal Asynchronous Receiver Transmitter (UART)

Transmission part (with parity bit)

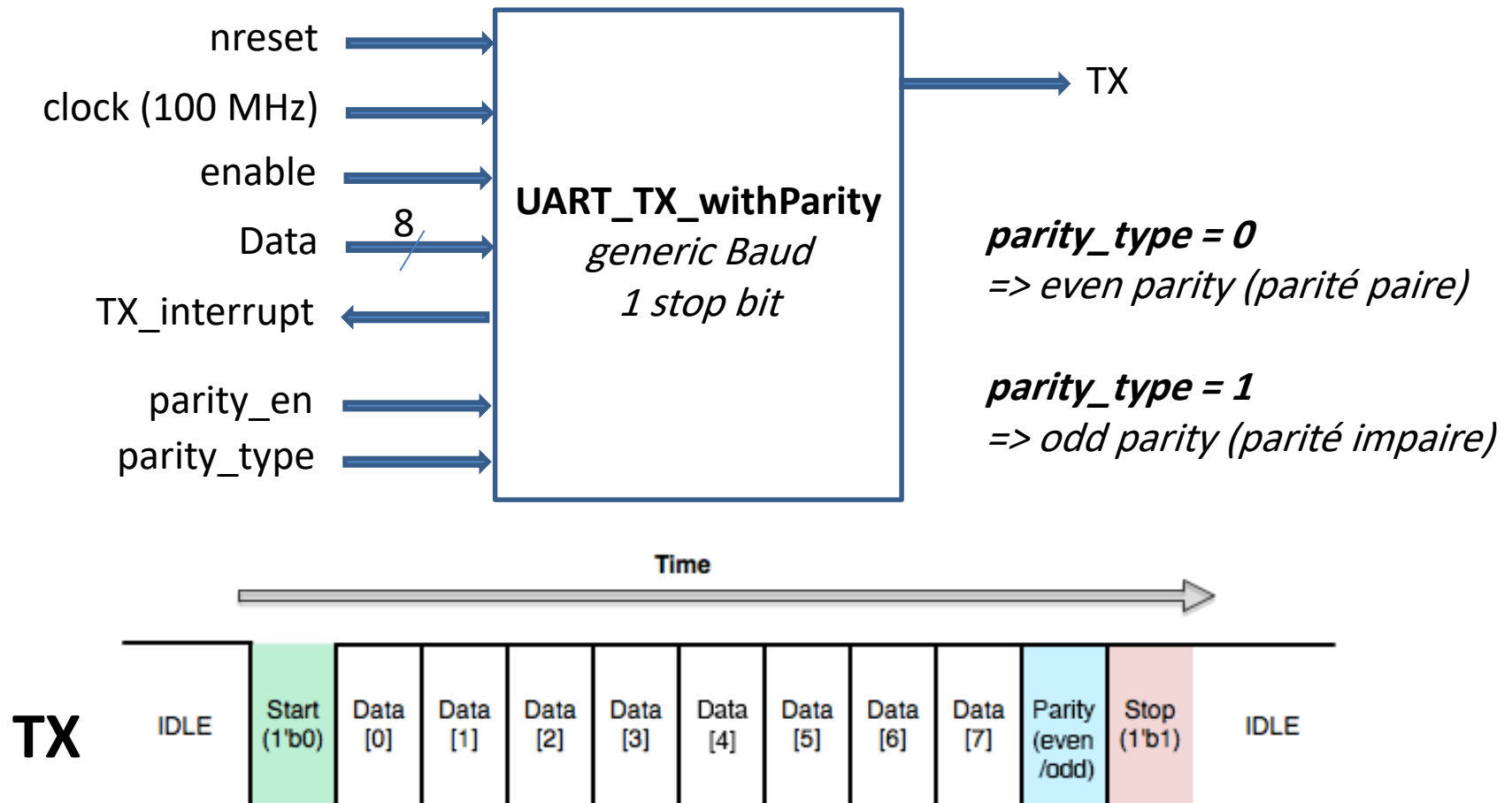


Digital circuit design examples using Xilinx Vivado

Design 5

Universal Asynchronous Receiver Transmitter (UART)

Transmission part (with parity bit)

7 bits of data	(count of 1 bits)	8 bits including parity	
		even	odd
0000000	0	00000000	00000001
1010001	3	10100011	10100010
1101001	4	11010010	11010011
1111111	7	11111111	11111110

 


Digital circuit design examples using Xilinx Vivado

Design 5

Universal Asynchronous Receiver Transmitter (UART)

Transmission part (with parity bit)

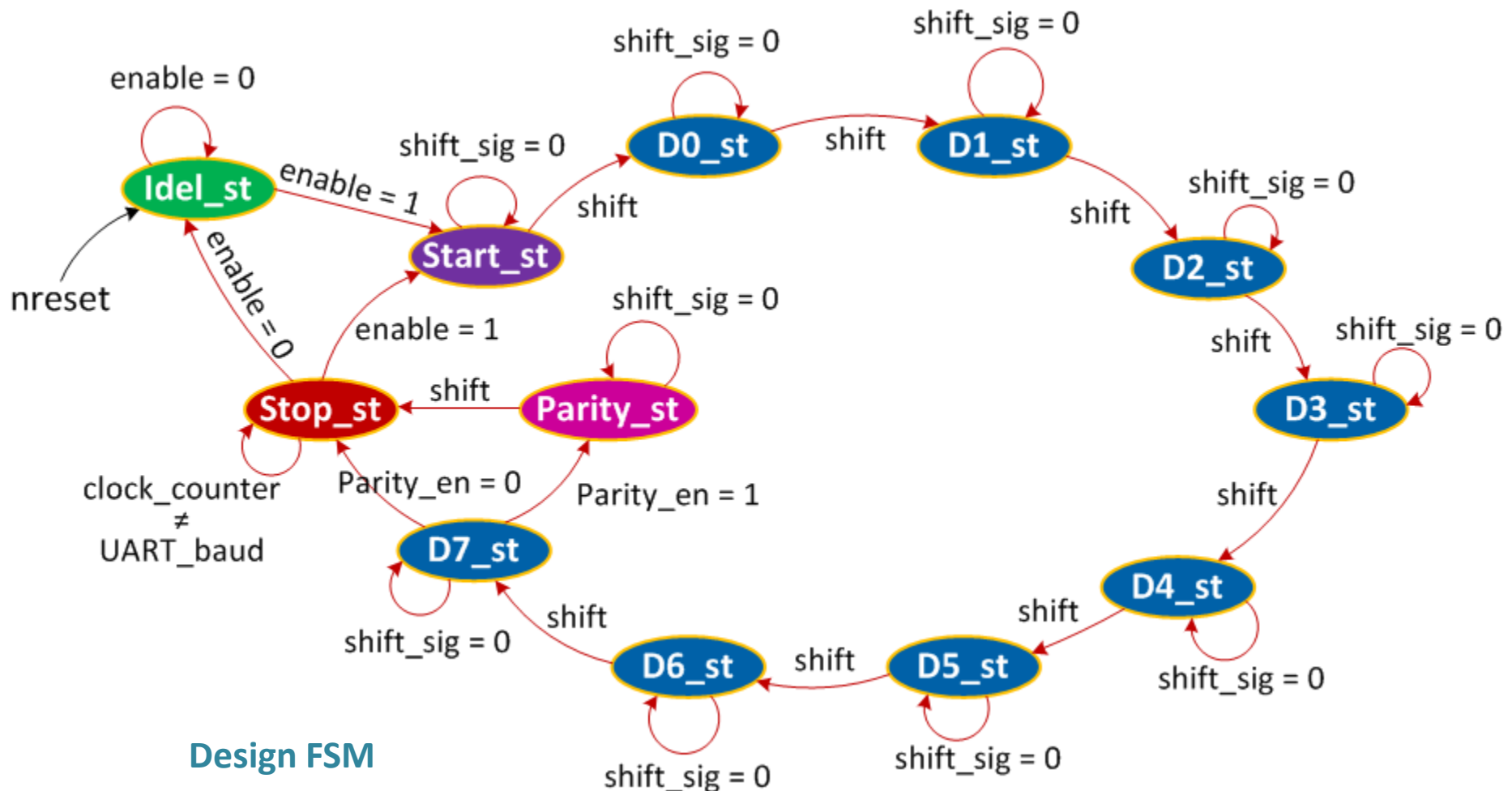


Digital circuit design examples using Xilinx Vivado

Design 5

Universal Asynchronous Receiver Transmitter (UART)

Transmission part (with parity bit)

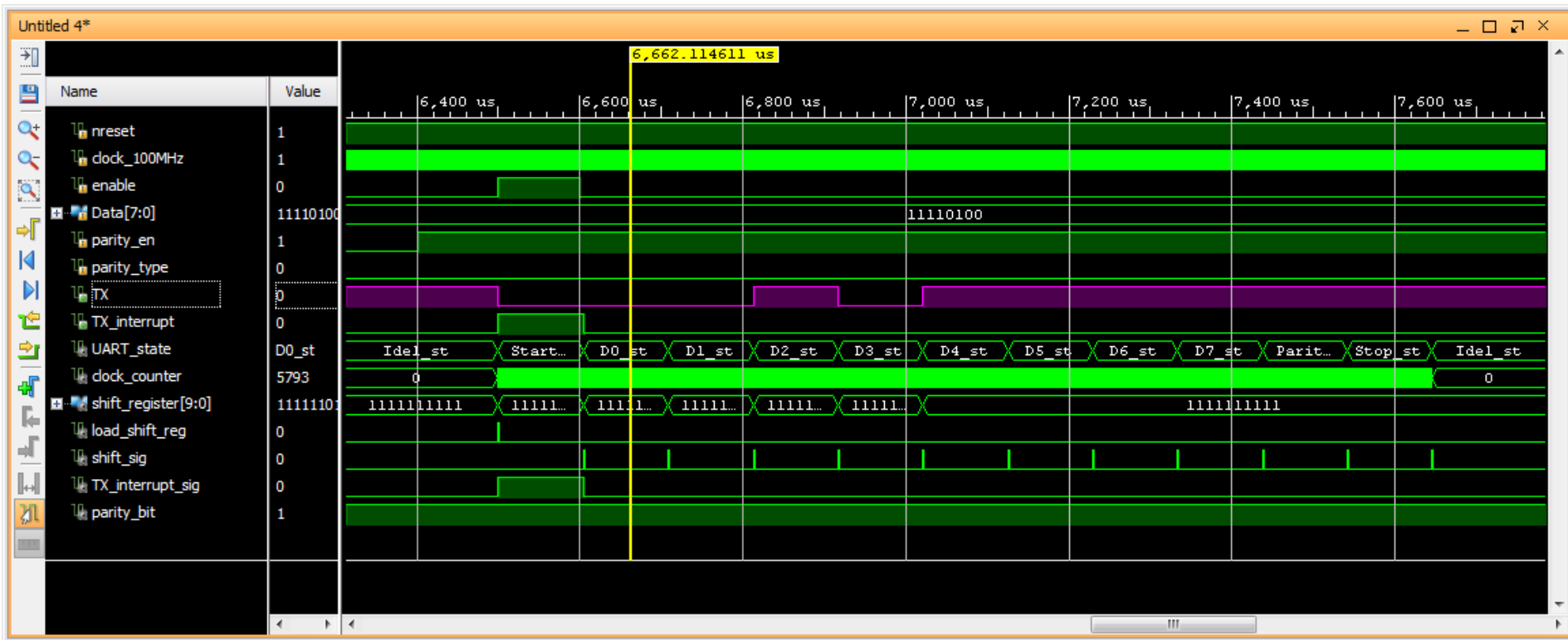

Simulation